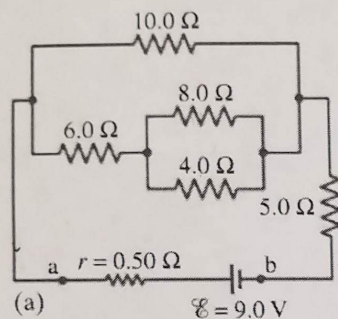


NAME:


SECTION:

1.




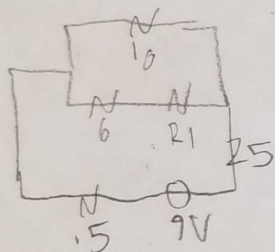**EXAMPLE 19-7 Analyzing a circuit.** A 9.0-V battery whose internal resistance  $r$  is  $0.50\ \Omega$  is connected in the circuit shown in Fig. 19-10a. (a) How much current is drawn from the battery? (b) What is the terminal voltage of the battery? (c) What is the current in the  $6.0\text{-}\Omega$  resistor?


**APPROACH** To find the current out of the battery, we first need to determine the equivalent resistance  $R_{eq}$  of the entire circuit, including  $r$ , which we do by identifying and isolating simple series or parallel combinations of resistors. Once we find  $I$  from Ohm's law,  $I = \mathcal{E}/R_{eq}$ , we get the terminal voltage using  $V_{ab} = \mathcal{E} - Ir$ . For (c) we apply Ohm's law to the  $6.0\text{-}\Omega$  resistor.



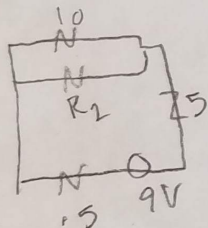
$$R_1 = \left[ \frac{1}{8\ \Omega} + \frac{1}{4\ \Omega} \right]^{-1} = \left[ \frac{3}{8\ \Omega} \right]^{-1} = 2.7\ \Omega$$


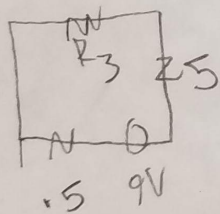
$$R_2 = 6\ \Omega + 2.7\ \Omega = 8.7\ \Omega$$


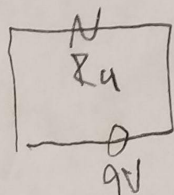
$$R_3 = R_2 + 5\ \Omega + 0.5\ \Omega = 10.3\ \Omega$$




$$I = \frac{9\text{ V}}{10.3\ \Omega} = 0.87\text{ A} \quad (a)$$

$$(b) V_{\text{terminal}} = 9\text{ V} - I(0.5\ \Omega) = 8.6\text{ V}$$

$$(c) I_{6\ \Omega} = \frac{9\text{ V} - (0.87\text{ A})(0.5\ \Omega + 5\ \Omega)}{8.7\ \Omega} = 0.49\text{ A}$$

Ex 19.8

2. Calculate  $I_1, I_2, I_3$ .

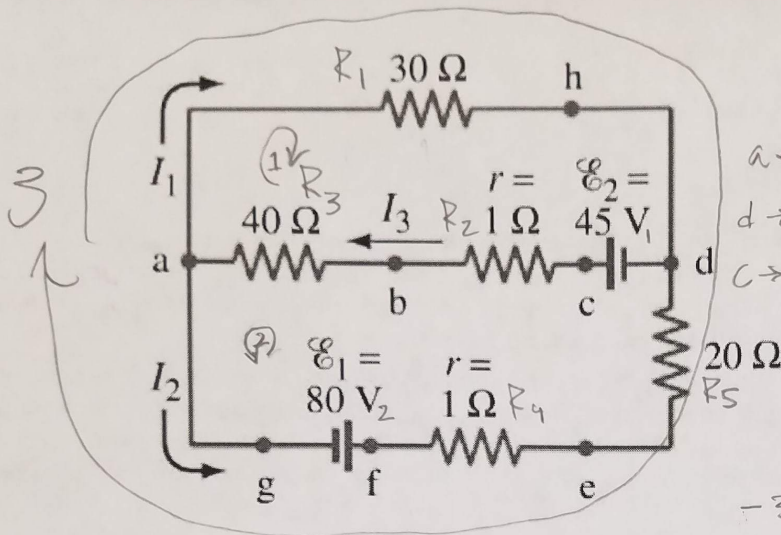

$$\textcircled{1} \quad I_3 = I_1 + I_2$$

$$\begin{aligned} a \leftrightarrow h: -(30\Omega) I_1 &= V_{ha} \\ d \rightarrow c: +45V &= V_{cd} \\ c \rightarrow a: -[(1+40)\Omega] I_3 &= V_{ac} \end{aligned}$$

$$\sum_{\text{loop 1}} V_{ij} = V_{ha} + V_{cd} + V_{ac} = 0$$

$$-30I_1 + 45 - 41I_3 = 0$$

$$\textcircled{1} \quad \sum_{\text{loop 1}} V_{ij} = V_{ha} + V_{cd} + V_{ac} = -R_1 I_1 + V_1 - (R_2 + R_3) I_3 = 0$$

$$\textcircled{2} \quad \sum_{\text{loop 2}} V_{ij} = V_{ga} + V_{fg} + V_{ef} = 0 + V_2 - R_4 I_2 - R_5 I_2 + V_1 - (R_2 + R_3) I_3$$

$$\textcircled{2} - \textcircled{1} = R_1 I_1 - V_1 + V_2 - I_2 (R_4 + R_5) = 0 \rightarrow I_2 = \frac{1}{R_4 + R_5} [V_2 + R_1 I_1]$$

$$\textcircled{1} \quad I_3 = I_1 + I_2 = I_1 + \frac{1}{R_4 + R_5} V_2 + \frac{R_1}{R_4 + R_5} I_1 = \left(1 + \frac{R_1}{R_4 + R_5}\right) I_1 + \frac{V_2}{R_4 + R_5}$$

$$\textcircled{1} \quad = \frac{1}{R_2 + R_3} [V_1 - R_1 I_1] = \frac{V_1}{R_2 + R_3} - \frac{R_1 I_1}{R_2 + R_3} \Rightarrow \frac{\frac{V_1}{R_2 + R_3} - \frac{V_2}{R_4 + R_5}}{1 + R_1 \left(\frac{1}{R_2 + R_3} + \frac{1}{R_4 + R_5}\right)} = I_1$$

$$\textcircled{3}: -I_1 R_1 + (R_5 + R_4) I_2 - V_2 = 0 \rightarrow I_2 = \frac{1}{R_4 + R_5} [V_2 + I_1 R_1]$$

$$\textcircled{1}: I_3 = I_1 + I_2$$

$$V_{ad} = -(48\Omega) I_3 + 45 \rightarrow -34.2V$$

$$V_2 - I_2 R_4 =$$